



**International Institute of Information Technology,  
Bangalore**

**Sizing of a Low Dropout Voltage Regulator (LDO)**

**Final Project for**

**Analog CMOS VLSI Design (VL502)**

Done By:-

Aditya R Venkateshwaran	MT2024502
Tushar Katole	MT2024518
Tanaya Mehta	MT2024537

Submitted to:-

Prof. Sakshi Arora

Assistant Professor,

International Institute of Information Technology - Bangalore

# 1. Specifications

**Instructions:** All specifications used in the design.

Table 1: Specifications Summary

Parameter	Value
V <sub>in</sub>	1.4
V <sub>out</sub>	1
PSRR	60
I <sub>load</sub> (min)	2m
I <sub>load</sub> (max)	10m
C <sub>load</sub>	1u
I <sub>quiescent</sub>	50u
Transient duration	1

## 2. Purpose of an LDO

An LDO (Low Dropout Regulator) is a type of linear voltage regulator that provides a stable, low-noise output voltage while operating with a small difference (dropout voltage) between the input and output voltages. Its role in circuits is crucial for ensuring reliability and performance.

### Key Purposes of an LDO

- **Voltage Regulation:** Maintains a stable output voltage despite variations in input voltage or load current, ensuring consistent operation of sensitive electronic components.
- **Low Noise Power Supply:** Provides clean, low-ripple power, which is essential for noise-sensitive applications such as RF circuits, audio devices, and ADCs/DACs.
- **Load Current Stability:** Supports a range of load currents while maintaining stability, which is vital in circuits with dynamic power requirements.
- **Protection for Downstream Components:** Safeguards sensitive downstream components from voltage fluctuations and overvoltage conditions.
- **Power Efficiency at Low Dropout:** Operates efficiently when the difference between input and output voltage is minimal, reducing energy loss compared to traditional linear regulators.

### 3. Relevance of Techplots



We Include all techplots generated after Python postprocessing, there are 5 takeaways, and we share a schematic of how these techplots were obtained.



- **Github Link:** <https://github.com/TanayaMehta003/ACMOS<sub>P</sub>ROJECT<sub>1</sub>/tree/main>  
Technology node : 45 nm
- $f_T$  improves with shorter channel lengths, making circuits faster with scaling.
- Comparison of different FOMs at different lengths

Length (nm)	gmro	Id/w	ft (GHz)
45	8	170	180
90	50	100	65
270	155	50	13

Table 2: Comparison of different FOM at different lengths for NMOS

- In this project we have taken  $V_{ds}$  to be 0.4 mV, and we expect that to result in some error because the  $V_{ds}$  across every MOSFET might not be the same after sizing the circuit under a particular load. To solve this problem what we can do is generate differnt techplots for different values of  $V_{ds}$  such as  $V_{ds}=0.6v$   $V_{ds}=1v$   $V_{ds}=1.8v$
- So using  $V_{ds}$  of different volts will take care of change in load currents and the errors can be reduced.
- For this project we are using  $V_{ds}$  of only 0.4 V

  Figure 1: NMOS Techplots after Python postprocessing -  $I_D/W$ Figure 2: NMOS Techplots after Python postprocessing -  $g_m r_o$

 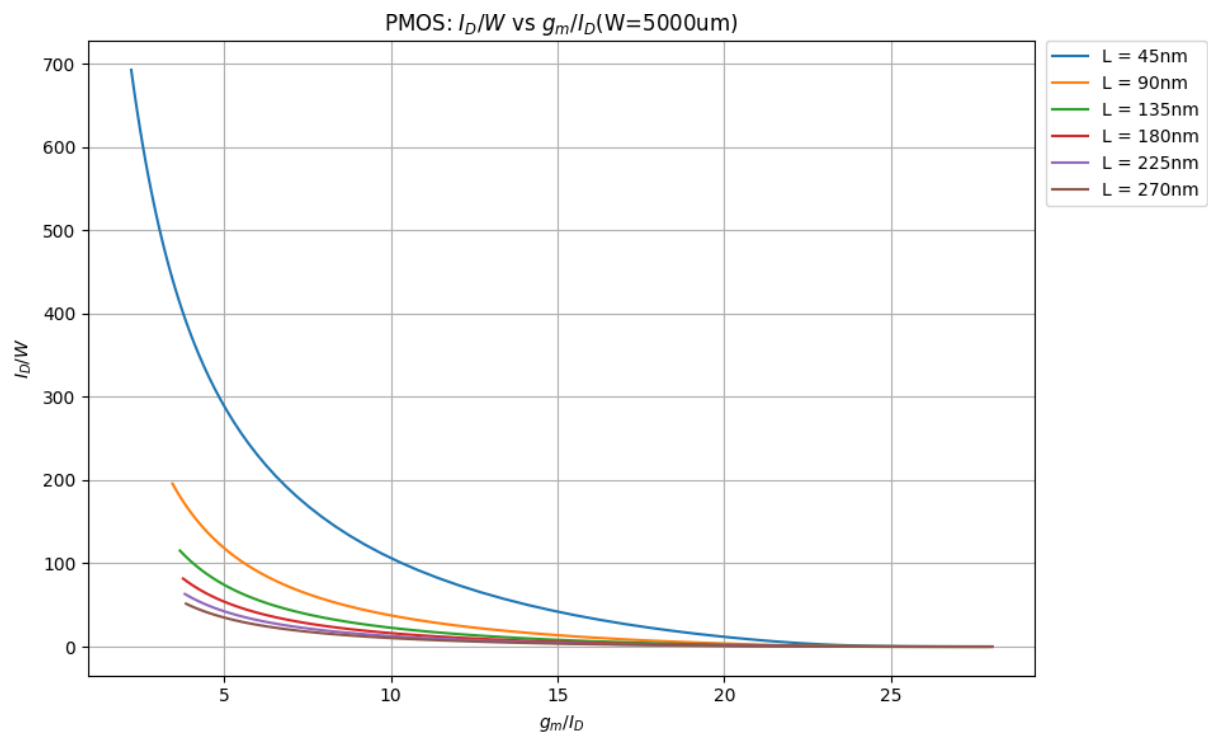Figure 3: NMOS Techplots after Python postprocessing -  $f_T$ Figure 4: PMOS Techplots after Python postprocessing -  $I_D/W$

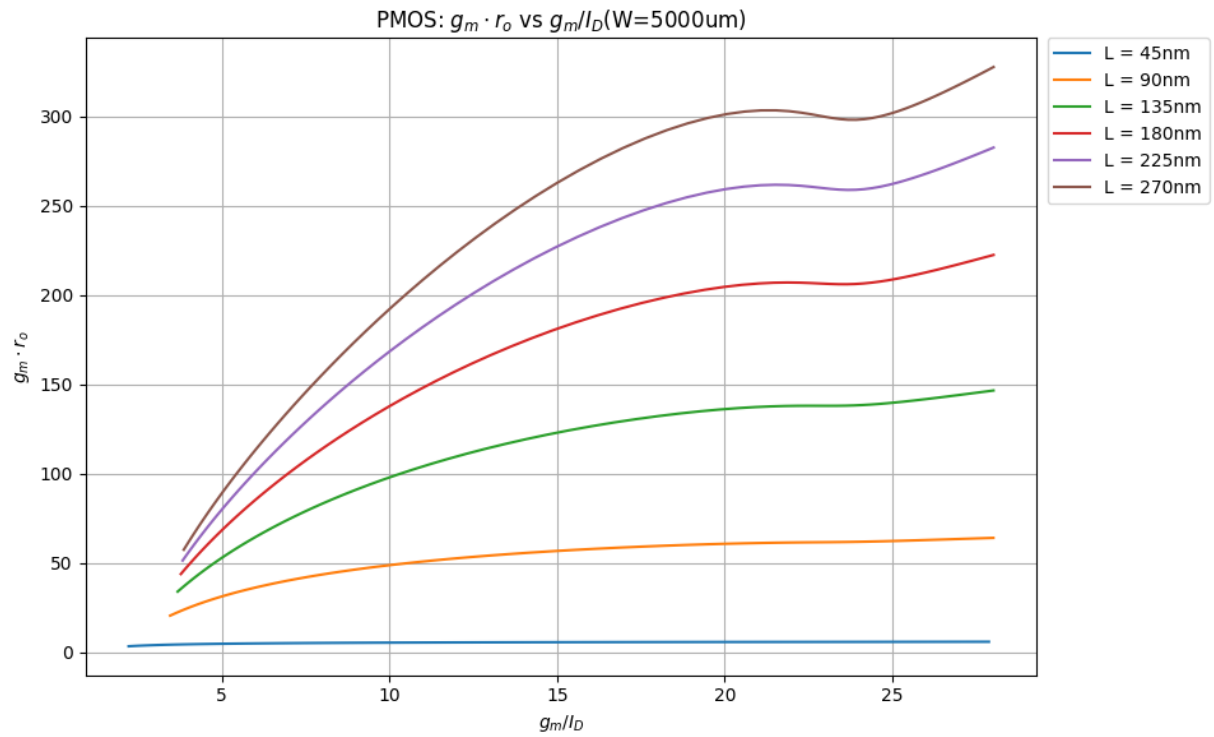


Figure 5: PMOS Techplots after Python postprocessing - gmro

 
Figure 6: PMOS Techplots after Python postprocessing -  $f_T$ 

Table 3: Key Differences Between 180nm and 45nm Technology Nodes for NMOS


Parameter	180nm Technology Node	45nm Technology Node
gmro	20	6.721
$I_d/W$ ( $\mu\text{A}/\mu\text{m}$ )	28	154.324
$f_T$ (Hz)	$1.6 \times 10^{10}$	$18.93 \times 10^{10}$

Table 4: Observations on Technology Scaling Effects

Parameter	Observation
gmro	As the channel length decreases, the output resistance ( $r_o$ ) decreases significantly, which dominates the intrinsic gain ( $gmro$ ). As a result, the overall value of $gmro$ decreases.
$I_d/W$	With reduced channel length, the drain current ( $I_d$ ) increases due to higher mobility and lower channel resistance. Consequently, $I_d/W$ increases, which is evident from the data.
$f_T$	A decrease in channel length increases the transconductance ( $g_m$ ), which directly leads to an increase in the unity-gain cutoff frequency ( $f_T$ ). This trend is observed in the values.

**We** Provide the sizes of the passFET, differential amplifier, and mirror transistors. here we also Include small-signal parameters and figures of merit (FOMs). Discuss loop gain under heavy and light load conditions.

Transistor	Size (W/L)	$g_m/I_d$	$g_m * r_o$	$I_d/W$	$f_t$
PassFET pmos	285.7u/90n	10	50	37	28 GHz
Diff-Amp pmos	675.67n/90n	10	40	37	28 GHz
Diff-Amp nmos	283n/90n	10	40	88.33	60 GHz
Current Mirror nmos	1080n/10u	-	-	40	10 GHz

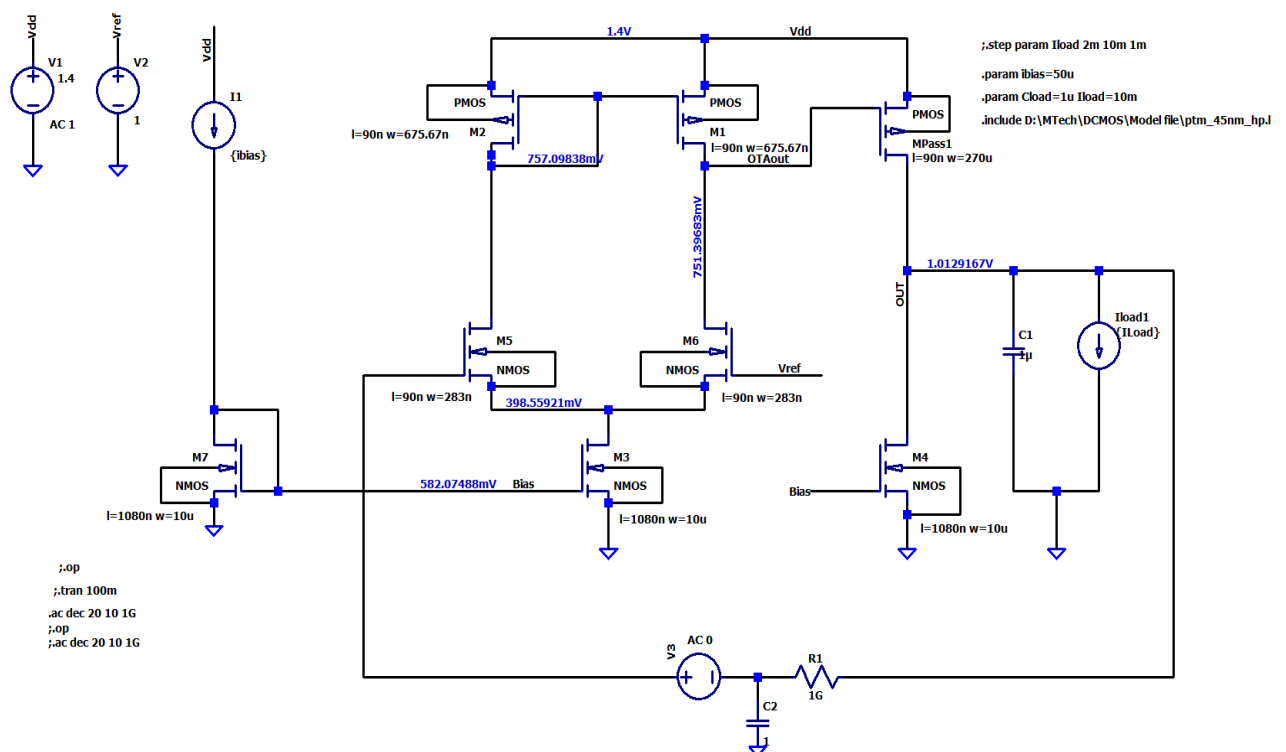

8



## 5. Stability Analysis

For Heavy load we get the following curve:

 


Figure 8: Stability Analysis for  $I=10$  mA

For Light load we get the following curve

 


Figure 9: Stability Analysis for  $I=2$  mA

From the above analysis we can see that the unity gain bandwidth is closer to the second pole for the heavy load case than the light load case. From the phase margin also we observe a smaller phase margin of 83.15 degrees for the heavy load case and 87.67 for light load case. From this analysis we can say that when we apply light load we get a more stable system.

Table 6: Key Metrics under Heavy and Light Load Conditions

Parameter	Heavy Load	Light Load
DC Loop Gain (dB)	58.6	62
Unity Gain Bandwidth (kHz)	401	105.09
Phase Margin (degrees)	83.15	87.67
Pole 1 (Hz)	401.27	105.09
Pole 2 (MHz)	2.83	13.45

## 6. PSRR Explanation

LDOs are essential components in the power supply of most ICs. They provide a ripple-free, stable fixed output voltage; isolating it from the input noise. An LDO has several important performance specifications and the power supply rejection ratio (PSRR) is one of them. PSRR is a quantitative measure of the attenuation of input ripples by the LDO at its output. These ripples can originate from various parts of the circuit, like DC/DC converters or shared power supplies of other circuit blocks. PSRR is expressed as  $PSRR = 20 * \log(V_{out}/V_{in})$ , where  $V_{out}$  and  $V_{in}$  refer to magnitudes of input and output ripples. In Figure 12, the PSRR of LDO is divided into two distinct regions:

- Region 1 covers the low and mid frequency range till the regulator bandwidth frequency (reg), where PSRR primarily depends on the loop gain (LG) of the regulator.
- Region 2 starts after reg, where PSRR is independent of LG and is dominated by output parasitics, PCB impedance, etc.

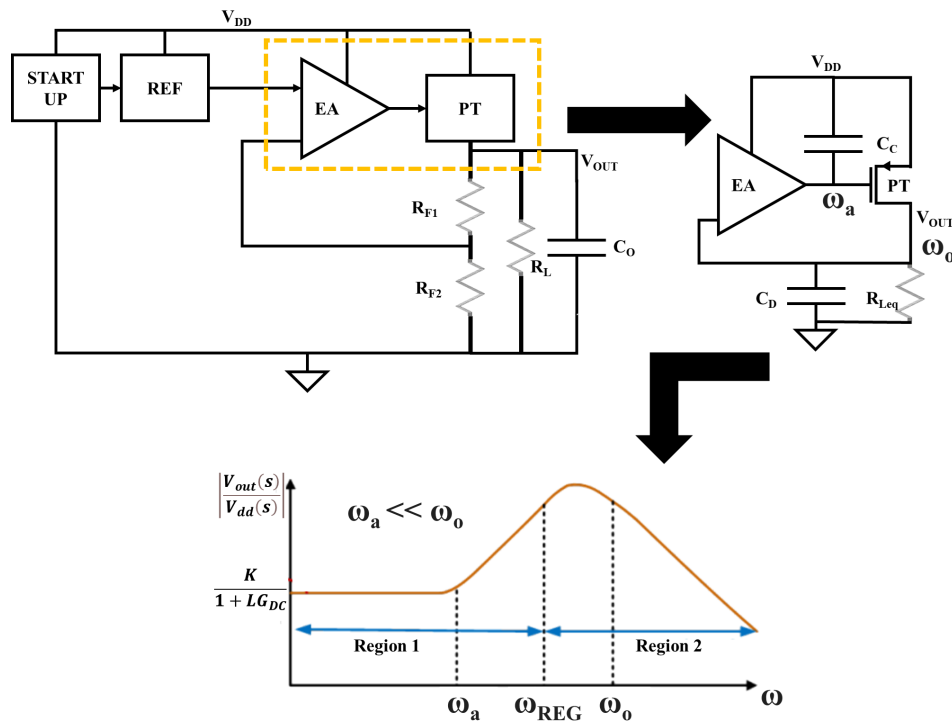


Figure 10: Block diagram of a low drop-out (LDO) regulator and its associated PSRR curve (linear scale)



## Output Log File:-

```

SPICE Output Log: D:\MTech\ACMOS\Project\TusharOLckt2.log
LTspice 24.0.12 for Windows
Circuit: * D:\MTech\ACMOS\Project\TusharOLckt2.asc
Start Time: Mon Dec 2 16:30:27 2024
solver = Normal
Maximum thread count: 8
tnom = 27
temp = 27
method = modified trap
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- BSIM4 MOSFETS ---
Name:      mpass1      m1      m2      m3      m4
Model:      pmos      pmos      pmos      nmos      nmos
Id:         -1.01e-02  -2.48e-05  -2.48e-05  4.97e-05  5.06e-05
Vgs:        -6.49e-01  -6.43e-01  -6.43e-01  5.82e-01  5.82e-01
Vds:        -3.87e-01  -6.49e-01  -6.43e-01  3.99e-01  1.01e+00
Vbs:         0.00e+00   0.00e+00   0.00e+00   0.00e+00   0.00e+00
Vth:        -4.87e-01  -4.84e-01  -4.84e-01  4.69e-01  4.69e-01
Vdsat:      -1.77e-01  -1.75e-01  -1.75e-01  1.38e-01  1.38e-01
Gm:          9.95e-02   2.50e-04   2.49e-04   6.06e-04   6.16e-04
Gds:         2.52e-03   5.00e-06   5.01e-06   1.93e-06   1.30e-06
Gmb:         2.11e-02   5.28e-05   5.28e-05   1.40e-04   1.42e-04
Cbd:         1.21e-13   2.86e-16   2.87e-16   4.48e-15   3.97e-15
Cbs:         2.16e-13   5.41e-16   5.41e-16   8.00e-15   8.00e-15

Name:      m5      m6      m7
Model:      nmos      nmos      nmos
Id:         2.48e-05  2.49e-05  5.00e-05
Vgs:         6.01e-01  6.01e-01  5.82e-01
Vds:         3.59e-01  3.53e-01  5.82e-01
Vbs:         0.00e+00  0.00e+00  0.00e+00
Vth:         4.66e-01  4.66e-01  4.69e-01
Vdsat:       1.43e-01  1.43e-01  1.38e-01
Gm:          2.44e-04  2.44e-04  6.10e-04
Gds:         5.07e-06  5.16e-06  1.48e-06
Gmb:         5.62e-05  5.63e-05  1.41e-04
Cbd:         1.28e-16  1.28e-16  4.30e-15
Cbs:         2.26e-16  2.26e-16  8.00e-15

Total elapsed time: 0.100 seconds.

```

Figure 12: Log File

From the above file we can verify that all the devices are in saturation as follows:

### Transistor Operating Regions Table

This document provides a table summarizing the operating regions of several transistors based on their parameters.

Table 7: All MOSFETs in saturation

Device Name	Device Type	$ V_{ds} $	$ V_{gs} $	$ V_t $	$ V_{gs}  -  V_t $	Reason for saturation
MPass1	PMOS	0.38	0.649	0.48	0.16	$V_{sd} > 0.16$
M1	PMOS	0.64	0.643	0.48	0.163	$V_{sd} > 0.163$
M2	PMOS	0.643	0.643	0.48	0.163	$V_{sd} > 0.163$
M5	NMOS	0.359	0.601	0.468	0.133	$V_{ds} > 0.133$
M6	NMOS	0.353	0.601	0.468	0.133	$V_{ds} > 0.133$
M3	NMOS	0.399	0.582	0.468	0.114	$V_{ds} > 0.114$
M7	NMOS	0.582	0.582	0.468	0.114	$V_{ds} > 0.114$
M4	NMOS	1.01	0.582	0.468	0.114	$V_{ds} > 0.114$

## Output Waveform

 



Figure 13: Output Waveform Vout

The phase margin is **83.15**. The output voltage (Loop Gain) comes out to be close to **58.6 dB**. The formula for loop gain is  $A_{diff} * A_{pass}$  where:

- $A_{diff}$  is differential amplifier gain
- $A_{pass}$  is the passfet gain

## Case 2:- Open Loop PSRR Calculation

Schematic

 


Note:- Always observe the Vota output should be closer to 1v, the better it is for PSRR at the output as the Vsg value will be close to 0.

A Bode plot showing the output voltage  $V_{out}$  (volts) versus Frequency (Hz) on a logarithmic scale. The plot features a blue line representing the frequency response. The y-axis ranges from -2.00 to 0.00 volts, and the x-axis ranges from  $10^1$  to  $10^9$  Hz. The response is flat at approximately -0.1 V for frequencies below  $10^6$  Hz, then drops sharply to -2.00 V by  $10^8$  Hz.

Frequency (Hz)	$V_{out}$ (volts)
$10^1$	-0.1
$10^2$	-0.1
$10^3$	-0.1
$10^4$	-0.1
$10^5$	-0.1
$10^6$	-0.25
$10^7$	-1.75
$10^8$	-2.00
$10^9$	-2.00

15

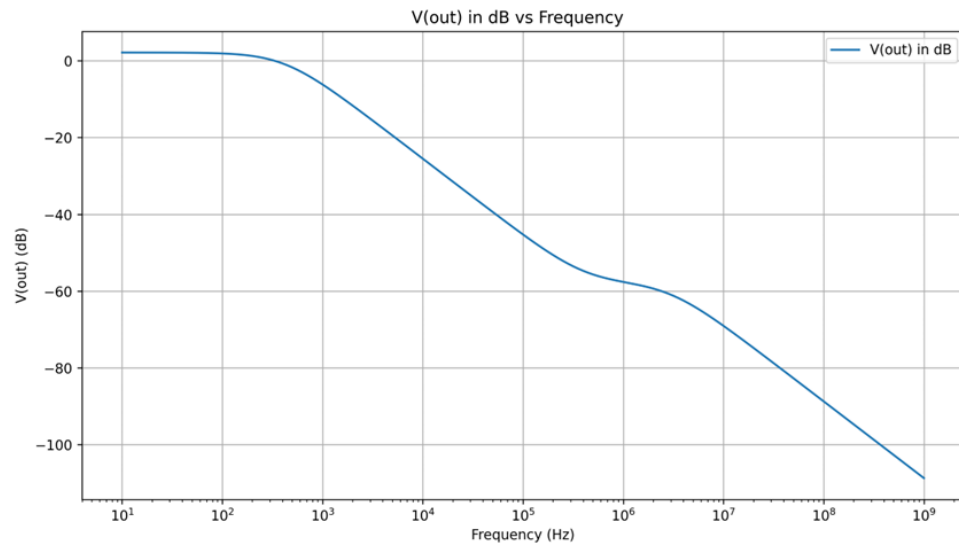Figure 16: Output Waveform  $V_{\text{out}}$



## Case 3:- Closed Loop PSRR Calculation

### Schematic

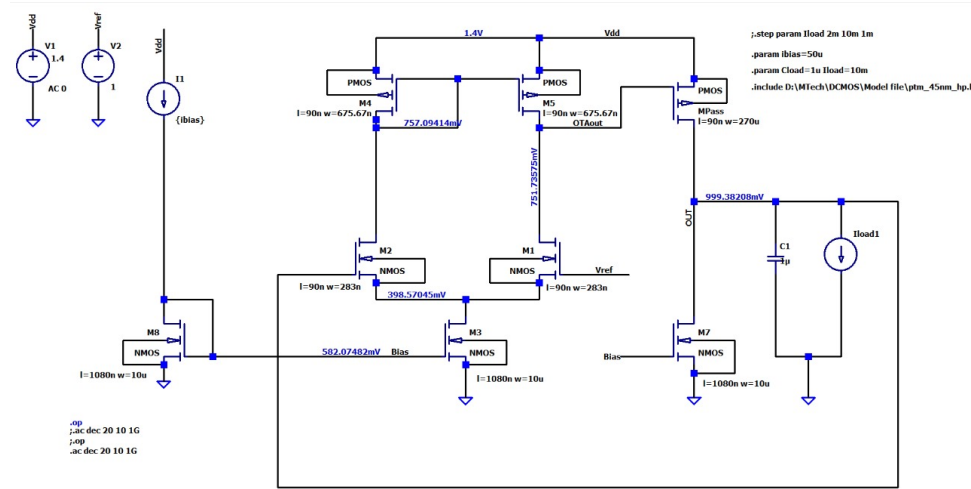


Figure 17: Schematic

**Explanation of the artifact used:-** In this case we can see that we have given a AC source in the voltage source VDD. We want to see the negative feedback in the circuit due to which we will get the output voltage cancelled out (small signal analysis). Here we should observe a high PSRR according to our specifications (60 dB) which tells us that our sizing is perfect. For this circuit we have given a feedback from the output terminal to the input of the diffamp which indicates the feedback path.

 
 


Figure 18: Output Waveform Vota

Figure 19: Output Waveform  $V_{\text{out}}$

## Light Load (2 mA)

### Case 1:- Loop Gain Analysis

#### Schematic

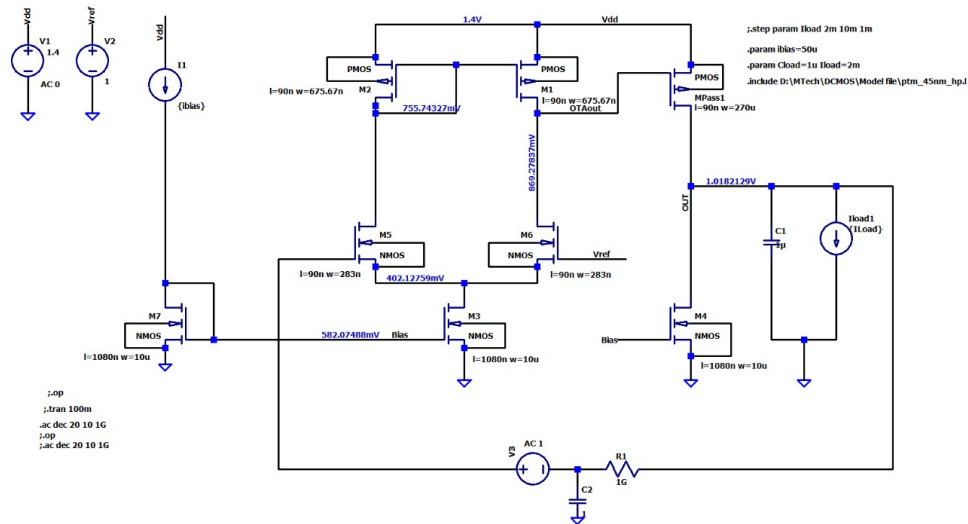


Figure 20: Schematic

## Output Log File:-

```

SPICE Output Log: D:\MTech\ACMOS\Project\TusharOLckt2.log
LTspice 24.0.12 for Windows
Circuit: * D:\MTech\ACMOS\Project\TusharOLckt2.asc
Start Time: Sat Dec 7 19:43:32 2024
solver = Normal
Maximum thread count: 8
tnom = 27
temp = 27
method = modified trap
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- BSIM4 MOSFETS ---
Name:      mpass1      m1      m2      m3      m4
Model:      pmos      pmos      pmos      nmos      nmos
Id:         -2.05e-03  -2.45e-05  -2.51e-05  4.97e-05  5.06e-05
Vgs:        -5.31e-01  -6.44e-01  -6.44e-01  5.82e-01  5.82e-01
Vds:        -3.82e-01  -5.31e-01  -6.44e-01  4.02e-01  1.02e+00
Vbs:         0.00e+00   0.00e+00   0.00e+00   0.00e+00   0.00e+00
Vth:        -4.87e-01  -4.85e-01  -4.84e-01  4.69e-01  4.69e-01
Vdsat:      -9.46e-02  -1.75e-01  -1.76e-01  1.38e-01  1.38e-01
Gm:          3.59e-02   2.47e-04   2.51e-04   6.06e-04   6.16e-04
Gds:          6.60e-04   5.24e-06   5.05e-06   1.91e-06   1.30e-06
Gmb:          7.41e-03   5.22e-05   5.32e-05   1.40e-04   1.42e-04
Cbd:          1.21e-13   2.94e-16   2.87e-16   4.47e-15   3.97e-15
Cbs:          2.16e-13   5.41e-16   5.41e-16   8.00e-15   8.00e-15

Name:      m5      m6      m7
Model:      nmos      nmos      nmos
Id:          2.51e-05   2.46e-05   5.00e-05
Vgs:          6.02e-01   5.98e-01   5.82e-01
Vds:          3.54e-01   4.67e-01   5.82e-01
Vbs:           0.00e+00   0.00e+00   0.00e+00
Vth:          4.66e-01   4.65e-01   4.69e-01
Vdsat:        1.44e-01   1.42e-01   1.38e-01
Gm:           2.45e-04   2.44e-04   6.10e-04
Gds:           5.19e-06   4.33e-06   1.48e-06
Gmb:           5.66e-05   5.63e-05   1.41e-04
Cbd:           1.28e-16   1.25e-16   4.30e-15
Cbs:           2.26e-16   2.26e-16   8.00e-15

Total elapsed time: 0.093 seconds.

```

Figure 21: Log File

## Transistor Operating Regions Table

This document provides a table summarizing the operating regions of several transistors based on their parameters.

Table 8: All MOSFETs in Saturation

Device Name	Device Type	$ V_{ds} $	$ V_{gs} $	$ V_t $	$ V_{gs}  -  V_t $	Reason for Saturation
MPass1	PMOS	0.382	0.531	0.487	0.044	$V_{sd} > 0.044$
M1	PMOS	0.531	0.644	0.485	0.159	$V_{sd} > 0.159$
M2	PMOS	0.644	0.644	0.484	0.160	$V_{sd} > 0.160$
M5	NMOS	0.354	0.602	0.466	0.136	$V_{ds} > 0.136$
M6	NMOS	0.467	0.598	0.465	0.133	$V_{ds} > 0.133$
M3	NMOS	0.402	0.582	0.469	0.113	$V_{ds} > 0.113$
M7	NMOS	0.582	0.582	0.469	0.113	$V_{ds} > 0.113$
M4	NMOS	1.020	0.582	0.469	0.113	$V_{ds} > 0.113$

 


Figure 22: Output Waveform Vout

The phase margin obtained is 87.58 degrees. This value is more than that of the value obtained for heavy load. Proving the point that for light load we get a better phase margin as the 1st pole and the 2nd pole are far apart.

## Case 2:- Open Loop PSRR Calculation

### Schematic

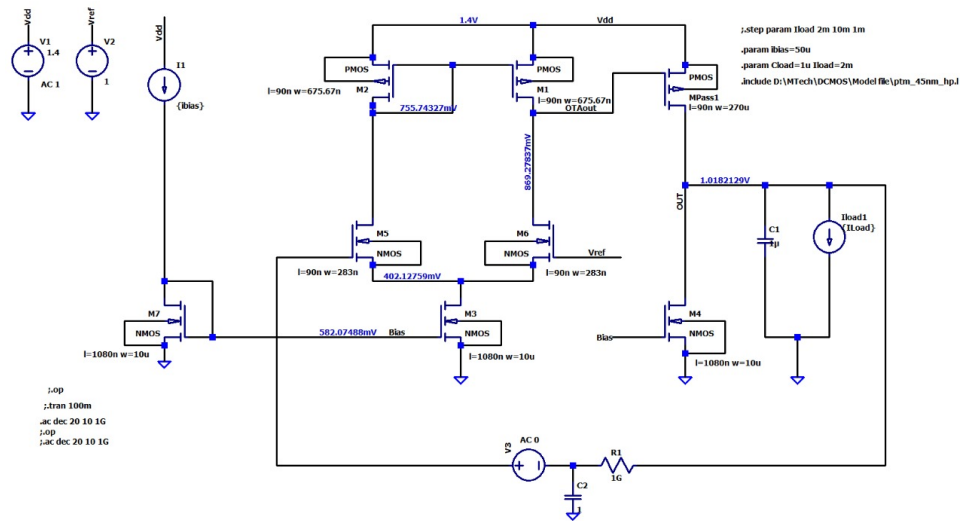


Figure 23: Schematic

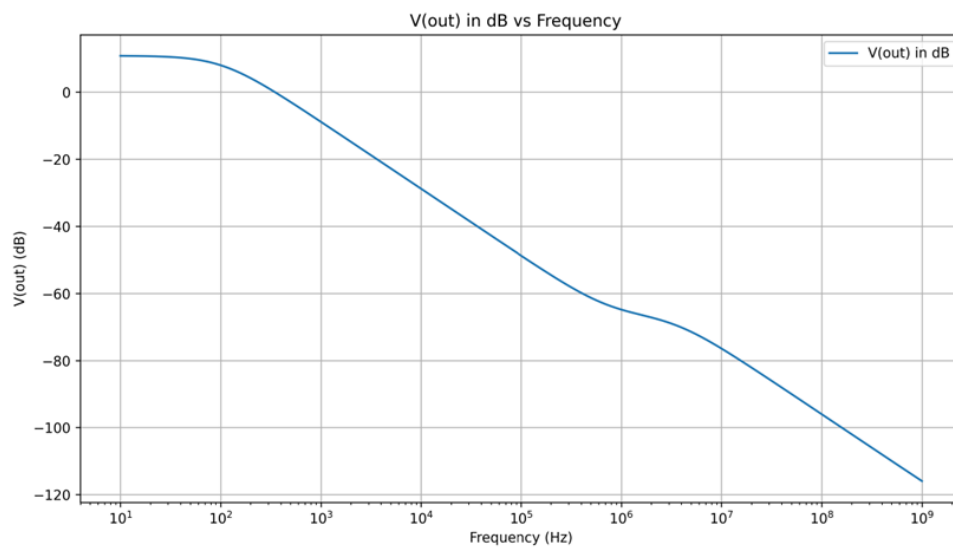


Figure 24: Output Waveform Vout

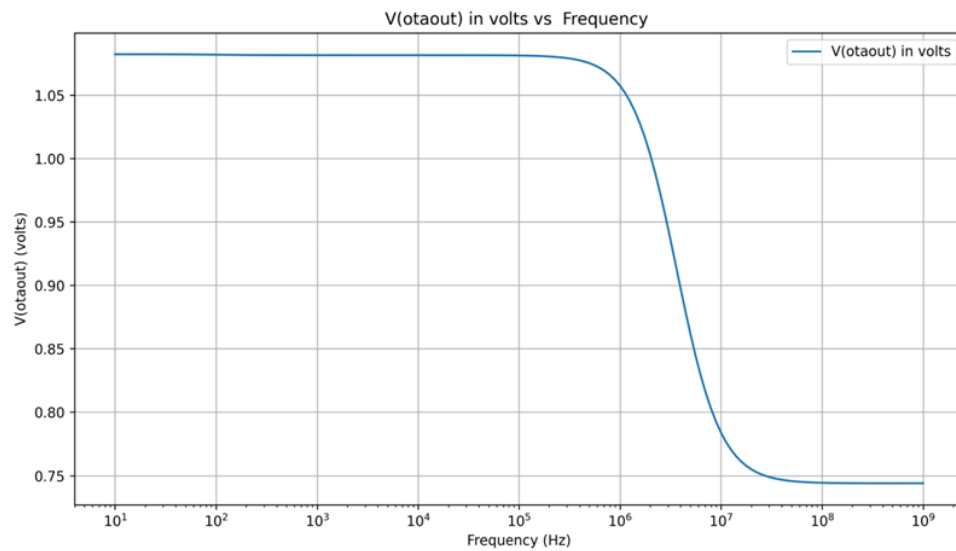


Figure 25: Output Waveform Vota

## Case 3:- Closed Loop PSRR Calculation

Schematic:

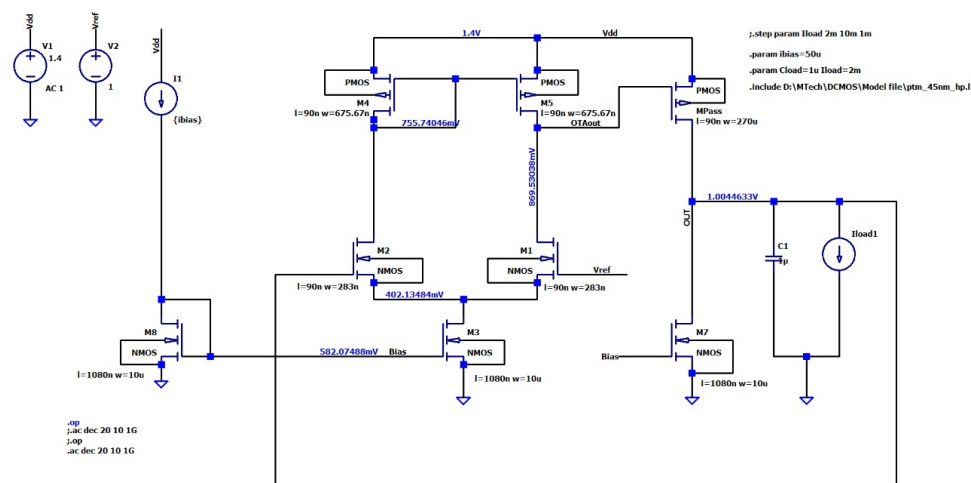


Figure 26: Schematic

 


Figure 27: Output Waveform Vout

 


Figure 28: Output Waveform Vota



## 8. Transient Simulation Results

We have given a pulse at the load with a rise time and fall time of 1u. Also the period of the pulse is 10m with a 50% duty cycle. From the below figure we can understand that the output is able to settle within the specified range of time. We are not able to observe any overshoot or undershoot in the output.

### Transient Analysis

#### Schematic

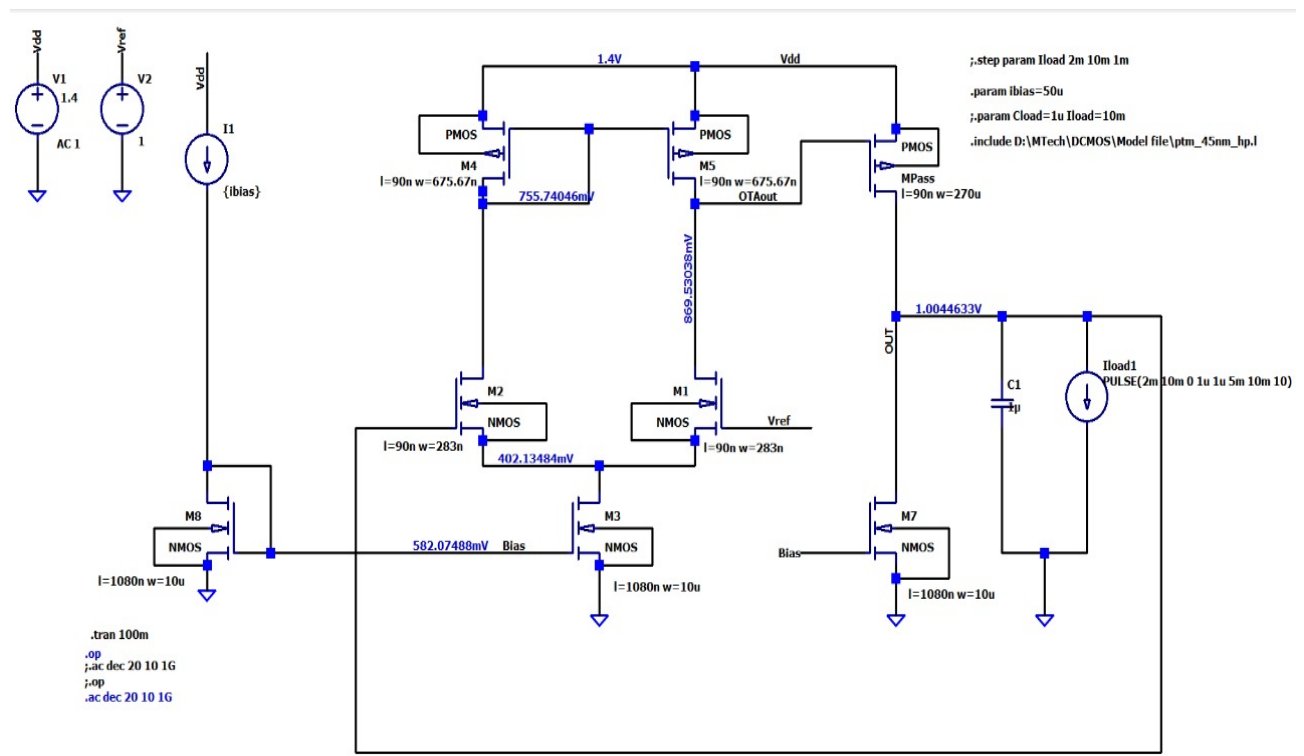
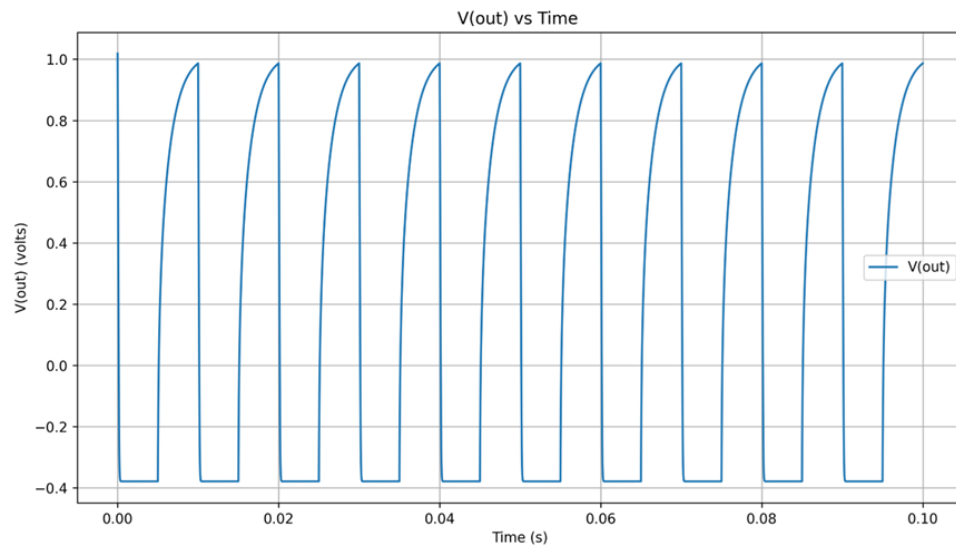
 


Figure 29: Schematic

Figure 30:  $V_{out}$  versus timeFigure 31:  $I_{load}$  versus time

## 9. Simulation vs. Hand Calculations

### For Heavy Load of Passfet

#### Hand Calculations:

- $r_o = 500 \Omega$
- $g_m = 0.1 \text{ A/V}$
- $W_{p1}$  (First Pole Location) = 2k
- $g_m r_o = 50$
- $C_L = 1u$
- $C_{gg} = 0.568p$

#### Simulation Results from SPICE Error Log:

- $r_o = 1/g_{ds} = 396.82 \Omega$
- $g_m = 0.0995 \text{ A/V}$
- $W_{p1}$  (first pole location) = 2.52k
- $g_m r_o = 39.48$

Table 9: Hand Calculation vs Simulation Results

Parameter	Hand Calculation	Simulation Result	% Difference
$r_o$ (ohm)	500.00	396.82	20.63%
$g_m$ (A/V)	0.1	0.0995	0.5%
$g_m * r_o$	50	39.48	21.04%
$W_{p1}$ (Hz)	2k	2.52k	20.63%
$W_{p2}$ (Hz)	22.007M	17.82M	19.02%
$W_{ugb}$ (Hz)	2M	2.52M	20.63%
$r_{odiff}$ (ohm)	80k	99.304k	19.43%
$g_{mdiff}$ (A/V)	250u	250u	0%

Name	mpass	m1	m2	m3	m4	m5	m6	m7
Model	pmos	pmos	pmos	nmos	nmos	nmos	nmos	nmos
<b>Id</b>	-1.01E-02	-2.48E-05	-2.48E-05	4.97E-05	5.06E-05	2.48E-05	2.49E-05	5.00E-05
<b>Vgs</b>	-6.49E-01	-6.43E-01	-6.43E-01	5.82E-01	5.82E-01	6.01E-01	6.01E-01	5.82E-01
<b>Vds</b>	-3.87E-01	-6.49E-01	-6.43E-01	3.99E-01	1.01E+00	3.59E-01	3.53E-01	5.82E-01
<b>Vbs</b>	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
<b>Vth</b>	-4.87E-01	-4.84E-01	-4.84E-01	4.69E-01	4.69E-01	4.66E-01	4.66E-01	4.69E-01
<b>Vdsat</b>	-1.77E-01	-1.75E-01	-1.75E-01	1.38E-01	1.38E-01	1.43E-01	1.43E-01	1.38E-01
<b>Gm</b>	9.95E-02	2.50E-04	2.49E-04	6.06E-04	6.16E-04	2.44E-04	2.44E-04	6.10E-04
<b>Gds</b>	2.52E-03	5.00E-06	5.01E-06	1.93E-06	1.30E-06	5.07E-06	5.16E-06	1.48E-06
<b>Gmb</b>	2.11E-02	5.28E-05	5.28E-05	1.40E-04	1.42E-04	5.62E-05	5.63E-05	1.41E-04
<b>Cbd</b>	1.21E-13	2.86E-16	2.87E-16	4.48E-15	3.97E-15	1.28E-16	1.28E-16	4.30E-15
<b>Cbs</b>	2.16E-13	5.41E-16	5.41E-16	8.00E-15	8.00E-15	2.26E-16	2.26E-16	8.00E-15
<b>rds</b>	3.97E+02	2.00E+05	2.00E+05	5.18E+05	7.69E+05	1.97E+05	1.94E+05	6.76E+05
<b>gm*rds</b>	3.95E+01	5.00E+01	4.97E+01	3.14E+02	4.74E+02	4.81E+01	4.73E+01	4.12E+02

Table 10: Transistor Parameters

## For Light Load of Passfet

### Hand Calculation

- $r_o = 2500 \Omega$
- $g_m = 0.02 \text{ A/V}$
- $W_{p1}$  (first pole location) = 400
- $g_m r_o = 50$
- $C_L = 1u$
- $C_{gg} = 0.1136p$

### Simulation Results from SPICE Error Log:

- $r_o = 1/g_{ds} = 1515.15 \Omega$
- $g_m = 0.0359 \text{ A/V}$
- $W_{p1}$  (first pole location) = 660
- $g_m r_o = 54.39$

Table 11: Hand Calculation vs Simulation Results

Parameter	Hand Calculation	Simulation Result	% Difference
$r_o$ (ohm)	2500.00	1515.15	39.39%
$g_m$ (A/V)	0.02	0.0359	44.28%
$g_m * r_o$	50	54.39	8%
$W_{p1}$ (Hz)	400	660	39.3%
$W_{p2}$ (Hz)	109.93M	84.5M	23.1%
$W_{ugb}$ (Hz)	400k	660k	39.3%
$r_{odiff}$ (ohm)	80k	104.04k	23.1%
$g_{mdiff}$ (A/V)	250u	247u	1.2%

Parameter	mpass	m1	m2	m3	m4	m5	m6	m7
<b>Id</b>	-2.05E-03	-2.45E-05	-2.51E-05	4.97E-05	5.06E-05	2.51E-05	2.46E-05	5.00E-05
<b>Vgs</b>	-5.31E-01	-6.44E-01	-6.44E-01	5.82E-01	5.82E-01	6.02E-01	5.98E-01	5.82E-01
<b>Vds</b>	-3.82E-01	-5.31E-01	-6.44E-01	4.02E-01	1.02E+00	3.54E-01	4.67E-01	5.82E-01
<b>Vbs</b>	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
<b>Vth</b>	-4.87E-01	-4.85E-01	-4.84E-01	4.69E-01	4.69E-01	4.66E-01	4.65E-01	4.69E-01
<b>Vdsat</b>	-9.46E-02	-1.75E-01	-1.76E-01	1.38E-01	1.38E-01	1.44E-01	1.42E-01	1.38E-01
<b>Gm</b>	3.59E-02	2.47E-04	2.51E-04	6.06E-04	6.16E-04	2.45E-04	2.44E-04	6.10E-04
<b>Gds</b>	6.60E-04	5.24E-06	5.05E-06	1.91E-06	1.30E-06	5.19E-06	4.33E-06	1.48E-06
<b>Gmb</b>	7.41E-03	5.22E-05	5.32E-05	1.40E-04	1.42E-04	5.66E-05	5.63E-05	1.41E-04
<b>Cbd</b>	1.21E-13	2.94E-16	2.87E-16	4.47E-15	3.97E-15	1.28E-16	1.25E-16	4.30E-15
<b>Cbs</b>	2.16E-13	5.41E-16	5.41E-16	8.00E-15	8.00E-15	2.26E-16	2.26E-16	8.00E-15
<b>ro</b>	1.52E+03	1.91E+05	1.98E+05	5.24E+05	7.69E+05	1.93E+05	2.31E+05	6.76E+05
<b>gm*rds</b>	5.44E+01	4.71E+01	4.97E+01	3.17E+02	4.74E+02	4.72E+01	5.64E+01	4.12E+02

Table 12: Transistor Parameters

## Internally Compensated LDO

### 10. FET Sizes

We Provide the sizes of the passFET, differential amplifier, and mirror transistors. here we also Include small-signal parameters and figures of merit (FOMs). Discuss loop gain under heavy and light load conditions.

**The value of the capacitance for the internal capacitor is 24.96 pf**

Table 13: FET Sizes and Parameters

Transistor	Size (W/L)	$g_m/I_d$	$g_m * r_o$	$I_d/W$	$f_t$
PassFET pmos	285.7u/90n	10	50	37	28 GHz
Diff-Amp pmos	675.67n/90n	10	40	37	28 GHz
Diff-Amp nmos	283n/90n	10	40	88.33	60 GHz
Current Mirror nmos	1080n/10u	-	-	40	10 GHz

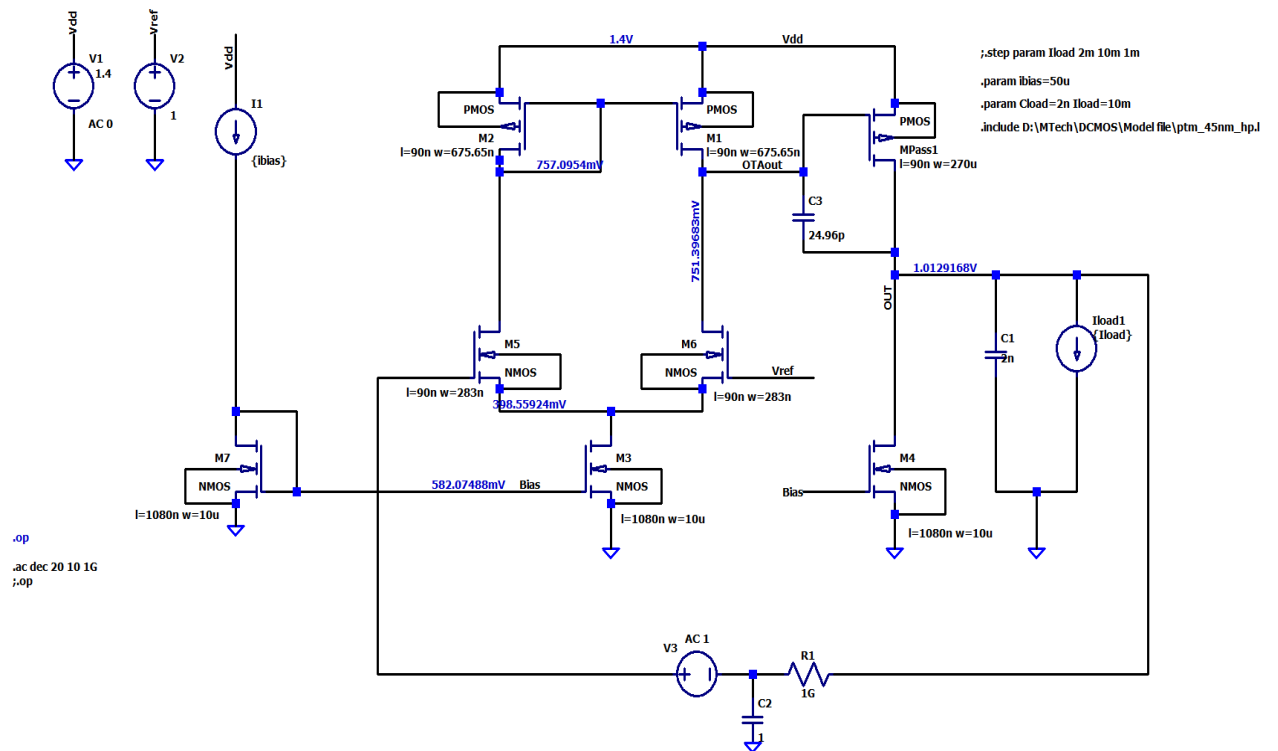


Figure 32: FET sizes and characteristics.

## 11. PSRR Simulation Result

### Heavy Load (10 mA)

### Case 1: Loop Gain Analysis


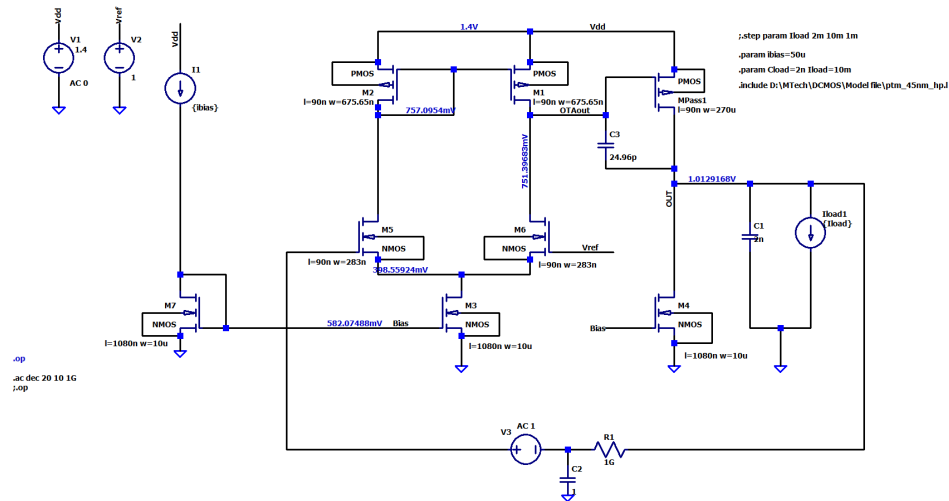


Figure 33: Schematic

## Output Log File:-

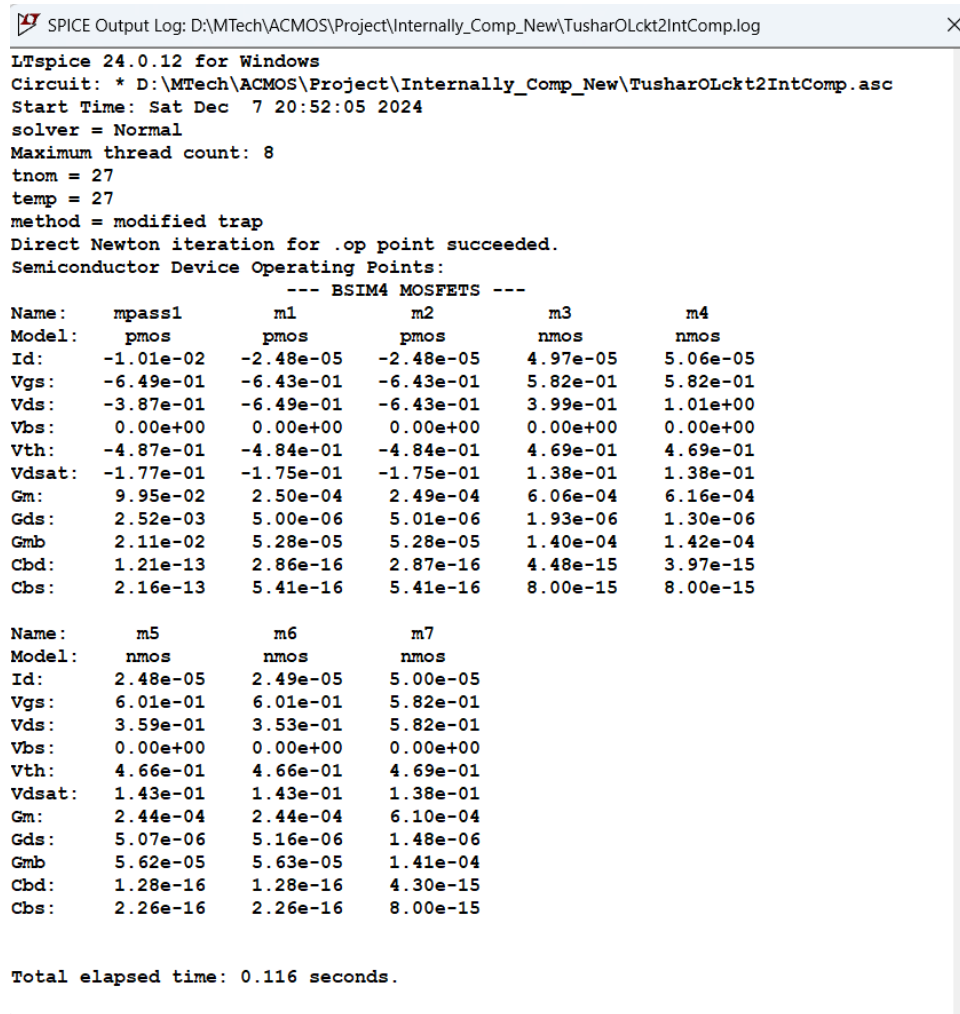

```

SPICE Output Log: D:\MTech\ACMOS\Project\Internally_Comp_New\TusharOLckt2IntComp.log
LTspice 24.0.12 for Windows
Circuit: * D:\MTech\ACMOS\Project\Internally_Comp_New\TusharOLckt2IntComp.asc
Start Time: Sat Dec 7 20:52:05 2024
solver = Normal
Maximum thread count: 8
tnom = 27
temp = 27
method = modified trap
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- BSIM4 MOSFETS ---
Name:      mpass1      m1      m2      m3      m4
Model:      pmos      pmos      pmos      nmos      nmos
Id:         -1.01e-02   -2.48e-05  -2.48e-05  4.97e-05  5.06e-05
Vgs:        -6.49e-01   -6.43e-01  -6.43e-01  5.82e-01  5.82e-01
Vds:        -3.87e-01   -6.49e-01  -6.43e-01  3.99e-01  1.01e+00
Vbs:         0.00e+00    0.00e+00   0.00e+00   0.00e+00  0.00e+00
Vth:        -4.87e-01   -4.84e-01  -4.84e-01  4.69e-01  4.69e-01
Vdsat:      -1.77e-01   -1.75e-01  -1.75e-01  1.38e-01  1.38e-01
Gm:          9.95e-02    2.50e-04   2.49e-04   6.06e-04  6.16e-04
Gds:         2.52e-03    5.00e-06   5.01e-06   1.93e-06  1.30e-06
Gmb:         2.11e-02    5.28e-05   5.28e-05   1.40e-04  1.42e-04
Cbd:         1.21e-13    2.86e-16   2.87e-16   4.48e-15  3.97e-15
Cbs:         2.16e-13    5.41e-16   5.41e-16   8.00e-15  8.00e-15

Name:      m5      m6      m7
Model:      nmos      nmos      nmos
Id:         2.48e-05   2.49e-05   5.00e-05
Vgs:         6.01e-01   6.01e-01   5.82e-01
Vds:         3.59e-01   3.53e-01   5.82e-01
Vbs:         0.00e+00   0.00e+00   0.00e+00
Vth:         4.66e-01   4.66e-01   4.69e-01
Vdsat:       1.43e-01   1.43e-01   1.38e-01
Gm:          2.44e-04   2.44e-04   6.10e-04
Gds:         5.07e-06   5.16e-06   1.48e-06
Gmb:         5.62e-05   5.63e-05   1.41e-04
Cbd:         1.28e-16   1.28e-16   4.30e-15
Cbs:         2.26e-16   2.26e-16   8.00e-15

Total elapsed time: 0.116 seconds.

```

Figure 34: Log File

Table 14: All MOSFETs in saturation

Device Name	Device Type	$ V_{ds} $	$ V_{gs} $	$ V_t $	$ V_{gs}  -  V_t $	Reason for saturation
MPass1	PMOS	0.38	0.649	0.48	0.16	$V_{sd} > 0.16$
M1	PMOS	0.64	0.643	0.48	0.163	$V_{sd} > 0.163$
M2	PMOS	0.643	0.643	0.48	0.163	$V_{sd} > 0.163$
M5	NMOS	0.359	0.601	0.468	0.133	$V_{ds} > 0.133$
M6	NMOS	0.353	0.601	0.468	0.133	$V_{ds} > 0.133$
M3	NMOS	0.399	0.582	0.468	0.114	$V_{ds} > 0.114$
M7	NMOS	0.582	0.582	0.468	0.114	$V_{ds} > 0.114$
M4	NMOS	1.01	0.582	0.468	0.114	$V_{ds} > 0.114$

## Output Waveform



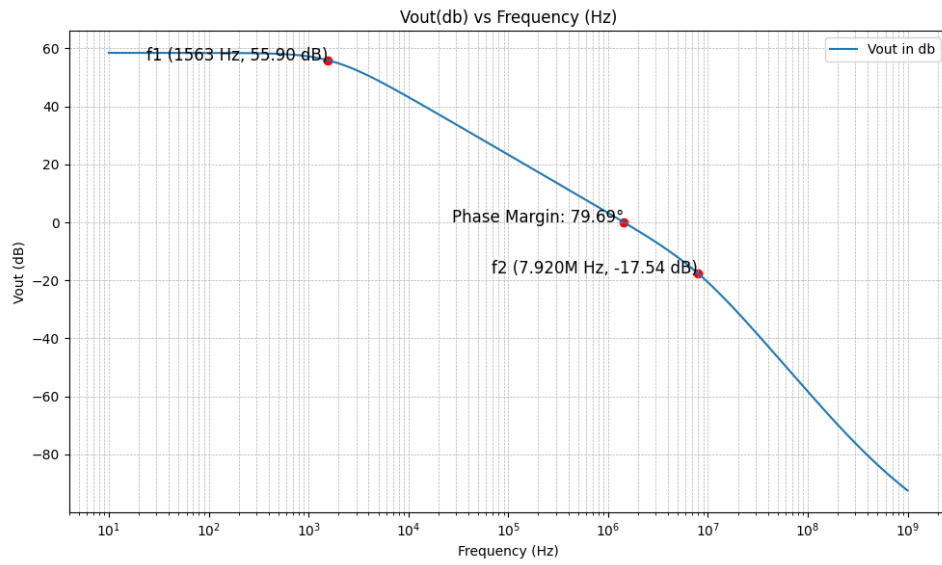


Figure 35: Output Waveform Vout

The phase margin is **79.69**.

## Case 2:- Open Loop PSRR calculation

Schematic:

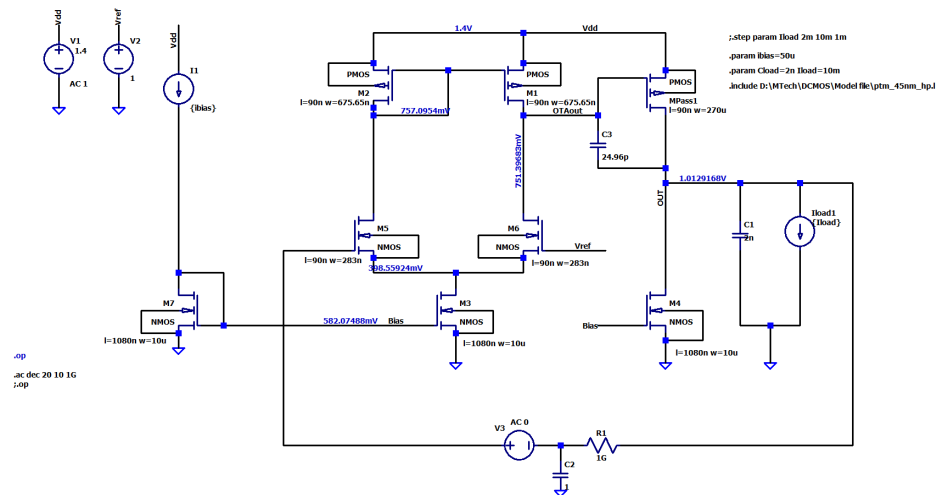


Figure 36: Schematic

Output Waveforms:

 


Figure 37: Output Waveform Vout

 


Figure 38: Output Waveform Vout

## Case 3:- Closed Loop PSRR Calculation

Schematic:

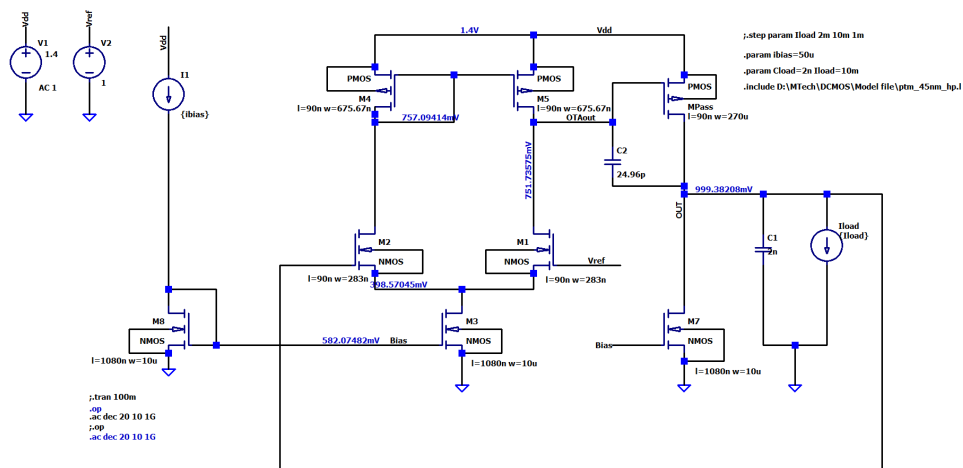


Figure 39: Schematic

Output Waveforms:

 


Figure 40: Output Waveform Vota

 


Figure 41: Output Waveform Vout

## Light Load (2 mA)

### Case 1: Loop Gain Analysis

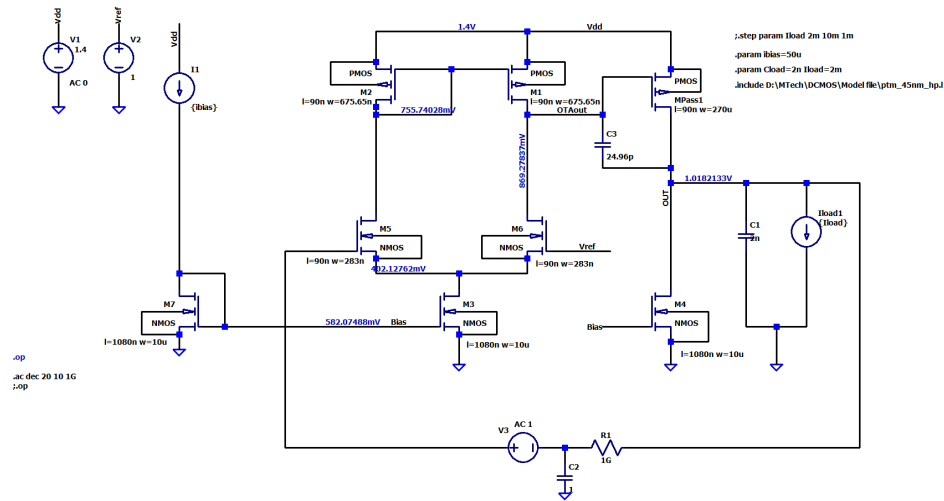


Figure 42: Schematic

## Output Log File:-

```

SPICE Output Log: D:\MTech\ACMOS\Project\TusharOLckt2.log
LTspice 24.0.12 for Windows
Circuit: * D:\MTech\ACMOS\Project\TusharOLckt2.asc
Start Time: Sat Dec 7 19:43:32 2024
solver = Normal
Maximum thread count: 8
tnom = 27
temp = 27
method = modified trap
Direct Newton iteration for .op point succeeded.
Semiconductor Device Operating Points:
--- BSIM4 MOSFETS ---
Name:      mpass1      m1      m2      m3      m4
Model:      pmos      pmos      pmos      nmos      nmos
Id:         -2.05e-03   -2.45e-05  -2.51e-05  4.97e-05  5.06e-05
Vgs:        -5.31e-01   -6.44e-01  -6.44e-01  5.82e-01  5.82e-01
Vds:        -3.82e-01   -5.31e-01  -6.44e-01  4.02e-01  1.02e+00
Vbs:         0.00e+00    0.00e+00    0.00e+00    0.00e+00    0.00e+00
Vth:        -4.87e-01   -4.85e-01  -4.84e-01  4.69e-01  4.69e-01
Vdsat:      -9.46e-02   -1.75e-01  -1.76e-01  1.38e-01  1.38e-01
Gm:          3.59e-02    2.47e-04    2.51e-04    6.06e-04    6.16e-04
Gds:          6.60e-04    5.24e-06    5.05e-06    1.91e-06    1.30e-06
Gmb:          7.41e-03    5.22e-05    5.32e-05    1.40e-04    1.42e-04
Cbd:          1.21e-13    2.94e-16    2.87e-16    4.47e-15    3.97e-15
Cbs:          2.16e-13    5.41e-16    5.41e-16    8.00e-15    8.00e-15

Name:      m5      m6      m7
Model:      nmos      nmos      nmos
Id:          2.51e-05   2.46e-05   5.00e-05
Vgs:          6.02e-01   5.98e-01   5.82e-01
Vds:          3.54e-01   4.67e-01   5.82e-01
Vbs:          0.00e+00    0.00e+00    0.00e+00
Vth:          4.66e-01   4.65e-01   4.69e-01
Vdsat:         1.44e-01   1.42e-01   1.38e-01
Gm:           2.45e-04    2.44e-04    6.10e-04
Gds:           5.19e-06    4.33e-06    1.48e-06
Gmb:           5.66e-05    5.63e-05    1.41e-04
Cbd:           1.28e-16    1.25e-16    4.30e-15
Cbs:           2.26e-16    2.26e-16    8.00e-15

Total elapsed time: 0.093 seconds.

```

Figure 43: Log File

## Transistor Operating Regions Table

This document provides a table summarizing the operating regions of several transistors based on their parameters.

Table 15: All MOSFETs in Saturation

Device Name	Device Type	$ V_{ds} $	$ V_{gs} $	$ V_t $	$ V_{gs}  -  V_t $	Reason for Saturation
MPass1	PMOS	0.382	0.531	0.487	0.044	$V_{sd} > 0.044$
M1	PMOS	0.531	0.644	0.485	0.159	$V_{sd} > 0.159$
M2	PMOS	0.644	0.644	0.484	0.160	$V_{sd} > 0.160$
M5	NMOS	0.354	0.602	0.466	0.136	$V_{ds} > 0.136$
M6	NMOS	0.467	0.598	0.465	0.133	$V_{ds} > 0.133$
M3	NMOS	0.402	0.582	0.469	0.113	$V_{ds} > 0.113$
M7	NMOS	0.582	0.582	0.469	0.113	$V_{ds} > 0.113$
M4	NMOS	1.020	0.582	0.469	0.113	$V_{ds} > 0.113$

## Output Waveform

 


Figure 44: Output Waveform Vout

The phase margin is **65.38**.





 


Figure 47: Output Waveform Vout

## Case 3:- Closed Loop PSRR Calculation

Schematic:

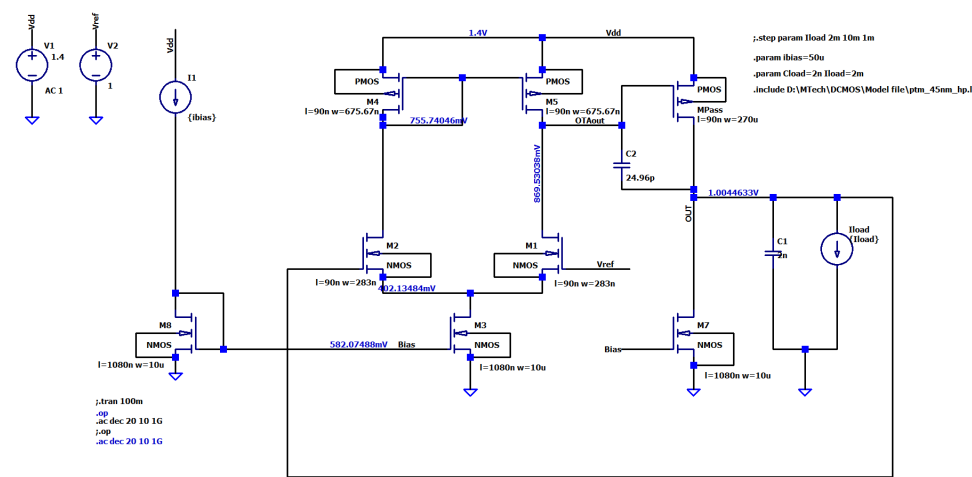


Figure 48: Schematic

Output Waveforms:

 


Figure 49: Output Waveform Vota


 
 


Figure 50: Output Waveform Vout

 

Figure 52:  $I_{load}Vstime$ Figure 53:  $V_{out}Vstime$

## 13. Simulation vs. Hand Calculations

### For Heavy Load of Passfet

#### Hand Calculations:

- $r_o = 500 \Omega$
- $g_m = 0.1 \text{ A/V}$
- $W_{p2}$  (Second Pole Location) = 10.33k
- $g_m r_o = 50$
- $C_L = 2n$
- $C_{gg} = 0.568p$

#### Simulation Results from SPICE Error Log:

- $r_o = 1/g_{ds} = 396.82 \Omega$
- $g_m = 0.0995 \text{ A/V}$
- $W_{p1}$  (First Pole Location) = 49.75M
- $g_m r_o = 39.48$

Table 16: Hand Calculation vs Simulation Results

Parameter	Hand Calculation	Simulation Result	% Difference
$r_o$ (ohm)	500.00	396.82	20.63%
$g_m$ (A/V)	0.1	0.0995	0.5%
$g_m * r_o$	50	39.48	21.04%
$W_{p1}$ (Hz)	10.33k	9.82k	4.9%
$W_{p2}$ (Hz)	50M	49.75M	0.5%
$W_{ugb}$ (Hz)	10.33M	9.82M	4.9%
$r_{odiff}$ (ohm)	80k	104.49k	23.4%
$g_{mdiff}$ (A/V)	250u	247u	1.2%

Name	mpass	m1	m2	m3	m4	m5	m6	m7
Model	pmos	pmos	pmos	nmos	nmos	nmos	nmos	nmos
<b>Id</b>	-1.01E-02	-2.48E-05	-2.48E-05	4.97E-05	5.06E-05	2.48E-05	2.49E-05	5.00E-05
<b>Vgs</b>	-6.49E-01	-6.43E-01	-6.43E-01	5.82E-01	5.82E-01	6.01E-01	6.01E-01	5.82E-01
<b>Vds</b>	-3.87E-01	-6.49E-01	-6.43E-01	3.99E-01	1.01E+00	3.59E-01	3.53E-01	5.82E-01
<b>Vbs</b>	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
<b>Vth</b>	-4.87E-01	-4.84E-01	-4.84E-01	4.69E-01	4.69E-01	4.66E-01	4.66E-01	4.69E-01
<b>Vdsat</b>	-1.77E-01	-1.75E-01	-1.75E-01	1.38E-01	1.38E-01	1.43E-01	1.43E-01	1.38E-01
<b>Gm</b>	9.95E-02	2.50E-04	2.49E-04	6.06E-04	6.16E-04	2.44E-04	2.44E-04	6.10E-04
<b>Gds</b>	2.52E-03	5.00E-06	5.01E-06	1.93E-06	1.30E-06	5.07E-06	5.16E-06	1.48E-06
<b>Gmb</b>	2.11E-02	5.28E-05	5.28E-05	1.40E-04	1.42E-04	5.62E-05	5.63E-05	1.41E-04
<b>Cbd</b>	1.21E-13	2.86E-16	2.87E-16	4.48E-15	3.97E-15	1.28E-16	1.28E-16	4.30E-15
<b>Cbs</b>	2.16E-13	5.41E-16	5.41E-16	8.00E-15	8.00E-15	2.26E-16	2.26E-16	8.00E-15
<b>rds</b>	3.97E+02	2.00E+05	2.00E+05	5.18E+05	7.69E+05	1.97E+05	1.94E+05	6.76E+05
<b>gm*rds</b>	3.95E+01	5.00E+01	4.97E+01	3.14E+02	4.74E+02	4.81E+01	4.73E+01	4.12E+02

Table 17: Transistor Parameters

## For Light Load of Passfet

### Hand Calculation

- $r_o = 2500 \Omega$
- $g_m = 0.02 \text{ A/V}$
- $W_{p1}$  (first pole location) = 10k
- $g_m r_o = 50$
- $C_L = 2n$
- $C_{gg} = 0.1136p$

### Simulation Results from SPICE Error Log:

- $r_o = 1/g_{ds} = 1515.15 \Omega$
- $g_m = 0.0359 \text{ A/V}$
- $W_{p1}$  (first pole location) = 7.07k
- $g_m r_o = 54.39$

Table 18: Hand Calculation vs Simulation Results

Parameter	Hand Calculation	Simulation Result	% Difference
$r_o$ (ohm)	2500.00	1515.15	39.39%
$g_m$ (A/V)	0.02	0.0359	33.33%
$g_m * r_o$	50	54.39	8%
$W_{p1}$ (Hz)	10k	7.07k	29.3%
$W_{p2}$ (Hz)	10M	17.95M	44.28%
$W_{ugb}$ (Hz)	10M	7.07M	29.3%
$r_{odiff}$ (ohm)	80k	104.04k	23.1%
$g_{mdiff}$ (A/V)	250u	250u	0%

Parameter	mpass	m1	m2	m3	m4	m5	m6	m7
<b>Id</b>	-2.05E-03	-2.45E-05	-2.51E-05	4.97E-05	5.06E-05	2.51E-05	2.46E-05	5.00E-05
<b>Vgs</b>	-5.31E-01	-6.44E-01	-6.44E-01	5.82E-01	5.82E-01	6.02E-01	5.98E-01	5.82E-01
<b>Vds</b>	-3.82E-01	-5.31E-01	-6.44E-01	4.02E-01	1.02E+00	3.54E-01	4.67E-01	5.82E-01
<b>Vbs</b>	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00	0.00E+00
<b>Vth</b>	-4.87E-01	-4.85E-01	-4.84E-01	4.69E-01	4.69E-01	4.66E-01	4.65E-01	4.69E-01
<b>Vdsat</b>	-9.46E-02	-1.75E-01	-1.76E-01	1.38E-01	1.38E-01	1.44E-01	1.42E-01	1.38E-01
<b>Gm</b>	3.59E-02	2.47E-04	2.51E-04	6.06E-04	6.16E-04	2.45E-04	2.44E-04	6.10E-04
<b>Gds</b>	6.60E-04	5.24E-06	5.05E-06	1.91E-06	1.30E-06	5.19E-06	4.33E-06	1.48E-06
<b>Gmb</b>	7.41E-03	5.22E-05	5.32E-05	1.40E-04	1.42E-04	5.66E-05	5.63E-05	1.41E-04
<b>Cbd</b>	1.21E-13	2.94E-16	2.87E-16	4.47E-15	3.97E-15	1.28E-16	1.25E-16	4.30E-15
<b>Cbs</b>	2.16E-13	5.41E-16	5.41E-16	8.00E-15	8.00E-15	2.26E-16	2.26E-16	8.00E-15
<b>ro</b>	1.52E+03	1.91E+05	1.98E+05	5.24E+05	7.69E+05	1.93E+05	2.31E+05	6.76E+05
<b>gm*rds</b>	5.44E+01	4.71E+01	4.97E+01	3.17E+02	4.74E+02	4.72E+01	5.64E+01	4.12E+02

Table 19: Transistor Parameters

## 14. Stability Analysis

For Heavy load we get the following curve:

 


Figure 54: Stability Analysis for I=10 mA

For Light load we get the following curve

 


Figure 55: Stability Analysis for I=2 mA



Table 20: Key Metrics under Heavy and Light Load Conditions

Parameter	Heavy Load	Light Load
DC Loop Gain (dB)	58.6	62
Unity Gain Bandwidth (MHz)	1.56	1.125
Phase Margin (degrees)	79.69	65.38
Pole 1 (kHz)	1.563	1.125
Pole 2 (MHz)	7.92	2.85

From the above analysis we can see that the unity gain bandwidth is closer to the second pole for the light load case than the light load case. From the phase margin also we can observe that we observe a lesser phase margin of 65.38 degrees for the light load case than that of the heavy load case. From this analysis, we can say that we get a more stable system when we apply heavy load.

## 15. Obsevation

- From the above analysis we can conclude that we need to design the LDO for higher current ratings in each case.
- Externally Compensated LDO is best for low load current as Phase Margin reduces with high load current.
- Internally Compensated LDO is best for high load current as Phase Margin reduces with low load current.